

1st Half

QP Code :552402

30/5/17

(3 Hours)

[Total Marks:80

N.B

1. Question No.1 is compulsory
2. Attempt any three question from remaining five questions
3. Assume suitable data wherever required but justify them
4. Draw appropriate waveforms wherever required

Extra

## 1. Solve any four

[20]

- (a) Explain Zener breakdown mechanism in Zener diode with VI characteristics.
- (b) Calculate the stability factor S for the fixed bias circuit with  $R_B=100K\Omega$ ,  $R_C = 1 K\Omega$ ,  $V_{BE}=0.7 V$  and  $V_{CE}=6 V$ .
- (c) What are the important features of a differential amplifier?
- (d) State De Morgan's Theorem and implement EX-OR gate using NAND gates only.
- (e) Convert T FF to D FF.

2. (a) Explain the working of Astable multivibrator using IC 555 with suitable waveforms. [10]
- (b) Design and implement one digit BCD adder using IC 7483. [10]

3. (a) Design a MOD-12 Asynchronous down counter. [10]
- (b) Define  $r_{ds}$ ,  $g_m$  and  $\mu$  for JFET and explain how to obtain them from characteristics. [10]

4. (a) Make subtraction using two's complement method  $(52)_{10} - (65)_{10}$  [5]
- (b) Simplify  $Y=ABC + BC'D + A'BC$  and realize using basic gates. [5]

(c) Explain how OPAMP can be used as summing, scaling and averaging amplifier in inverting configuration with derivation of output voltage equation. [10]

5. (a) Explain the working of LCD. [5]

(b) Define load regulation and Line regulation of power Supply. [5]

(c) Write in short about ENTITY declarations in VHDL. Write VHDL program for full adder. [10]

6. (a) Compare schottky barrier diode and PN junction diode. [5]

(b) Draw circuit diagram of voltage divider bias using CE configuration and explain how it stabilizes Operating point. [5]

(c) Implement the following Boolean function using only one 8:1 Mux and few gates  
 $F = \sum m(0,1,3,4,5,7,9,10,12,13,15)$  [5]

(d) Convert  $(101101.1101)_2$  to decimal, hexadecimal and octal form. [5]