

SE SEM-III CBGS IT NOV/DEC-2016

SUB:- ADC

16/12/2016

QP Code :552400

Extra

(3 Hours)

[Total Marks:80]

N.B.: (1) Question No. 1 is compulsory.

(2) Solve any three questions out of remaining five.

(3) Figures to right indicate full marks.

(4) Assume suitable data where necessary.

1. Attempt any five out of six questions

- What are the various regions that a transistor can operate? In which region can a transistor be operated if it is used as a switch?
- Give some applications of OpAmp and explain the block diagram of Op Amp.
- Explain the working of LCD.
- Minimize the following boolean expression using K-map

$$F(A,B,C,D) = \sum m(0,3,7,11,15) + d(1,2,5)$$

- Draw the truth table and excitation table for S-R flip flop.
- Convert $(101101.1101)_2$ to decimal, octal and hexa decimal.

- What is the need for biasing? Explain voltage divider bias and locate the Q points (10)
 - Draw the truth table for full adder and realize using 3:8 decoder (10)

- Explain the working of Monostable Multivibrator using IC555. Draw the waveforms and give its applications (10)
 - Design and implement one digit BCD adder using IC- 7483. (10)

- Design and implement binary to gray code converter (10)
 - Realize the following expression using only one 8:1 MUX and few logic gates (05)
 $F(A,B,C,D) = \sum m(0,3,6,8,11,13,15)$
 - Explain the practical differentiator circuit using op-Amp. (05)

- Explain differential amplifier and elaborate on any one method to improve the CMRR (10)
 - Design a half adder using VHDL (05)
 - Design mod-3 up counter using JK Flip Flop (05)

- Write short notes on any four (20)
 - Bidirectional shift registers
 - Full subtractor
 - Basic Logic Gates
 - BCD and Excess-3 code
 - JFET